

**VII. PROBLEMS:**

- 1) **An inductive circuit has a resistance of 2.0 Ohms in series with an inductance of 0.015 henry? Find (a) Current (b) power Factor (c) Power consumed? When connected across 200 Volts, 50 Hz. Supply mains?**

Ans Given data

$$R = 2.0 \text{ Ohms}, \quad L = 0.015$$

$$V = 200\text{V}, \quad f = 50 \text{ Hz.}$$

Formula used

$$Z = \sqrt{R^2 + X_L^2}$$

$$X_L = 2\pi f L$$

$$I = \frac{V}{Z}$$

$$\text{P.F} = \frac{R}{Z}$$

$$\text{Power} = VI \cos \phi \text{ (P.F)}$$

$$X_L = 2\pi \times 50 \times 0.015 = 4.714 \text{ Ohms.}$$

$$Z = \sqrt{(2)^2 + (4.714)^2} \\ = \sqrt{26.22} = 5.121 \text{ Ohms.}$$

$$(a) \quad I = V/Z = 200/5.121 = 39.05 \text{ Amps.}$$

$$(b) \quad \text{Power Factor} = \frac{R}{Z} = \frac{2}{5.121} = 0.39$$

$$(c) \quad \text{Power Consumed } P = VI \cos \phi \\ = 200 \times 39.05 \times 0.39 \\ = 3045.9 \text{ Watts.}$$

- 2) **Calculate the Line and Phase current of AC, 3 phase, 400 Volts, 7.5 B.H.P.? Motor with a power factor of 0.8 and efficiency 90%, when the winding is connected (a) in star (b) in Delta?**

Ans Given Data

$$V_L = 400 \text{ Volts, 3 Phase}$$

$$\text{BHP} = 7.5, \text{ P.F} = 0.8$$

$$\eta = 90\%$$

Formula used -

$$\text{Efficiency } \eta = \frac{\text{Output}}{\text{Input}} \text{ or Input} = \frac{\text{Output}}{\eta}$$

$$\text{Power } P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{BHP} = 7.5 \times 746 \text{ Watts.}$$

$$= 5595 \text{ Watts.}$$

$$\text{Input (P)} = \frac{\text{Output}}{\eta} = \frac{5595}{0.9}$$

$$P = 6216.66 \text{ Watts.}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$6216.66 = \sqrt{3} \times 400 \times I_L \times 0.8$$

$$I_L = \underline{6216.66}$$

$$\frac{\sqrt{3} \times 400 \times I_L \times 0.8}{\sqrt{3} \times 400 \times I_L \times 0.8}$$

$$I_L = 11.2 \text{ Amps.}$$

(a) In star Line current = Phase current

$$\text{Therefore } I_{ph} = 11.2 \text{ Amps.}$$

(b) In Delta Phase current

$$I_{ph} = I_L / \sqrt{3} = 11.2 / \sqrt{3} = 6.4 \text{ Amps.}$$

3) **A 250 KVA, 11000/400 Volts Delta / Star 3 phase transformer has load of 100 Amps. Find the line current on primary?**

Ans Given Data

$$\text{Primary Voltage } V_p = 11000 \text{ Volts}$$

$$\text{Secondary Voltage } V_s = 440 / \sqrt{3} \text{ (Since star connected)}$$

$$\text{Secondary Voltage } I_s = 100 \text{ Amps.}$$

$$\text{Power} = 250,000 \text{ VA}$$

$$\text{Formula : } V_s / I_s = I_p / I_s$$

$$\frac{440 / \sqrt{3}}{11,000} = \frac{I_p}{400}$$

$$\frac{440 / \sqrt{3}}{11,000} \times 100 = \frac{40}{11 \times \sqrt{3}}$$

$$= 2.09 \text{ Amp.}$$

4) **Find the diameter of copper wire in mm, if the resistance of 1.5 Kilometer wire is 7.2 Ohms? (Specific Resistance of copper is  $1.7 \times 10^{-6} \text{ Ohm/cm}^3$ )**

Ans Given Data

$$\text{Length} = 1.5 \text{ Km}$$

$$= 15,000 \text{ cm}$$

$$\text{Resistance} = 7.2 \text{ Ohms.}$$

$$\rho = \frac{1.7}{10^6} = 1.7 \times 10^{-6}$$

$$\text{We Know } R = \rho L/a$$

$$7.2 = 1.7 \times 10^{-6} \times 15,000 / a$$

$$a = 1.7 / 1,00,000 \times 15,000 / 7.2$$

$$= 0.035 \text{ sq.cm.}$$

$$\text{Now } a = \pi d^2 / 4$$

$$0.035 = \pi \times d^2 / 4$$

$$d = \sqrt{\frac{0.035 \times 4}{\pi}} = 0.21 \text{ cm.}$$

5) **Find the capacity of pump (HP) to pump the water at the rate of 20 Gallons per minute, from the bore well of 250 ft. depth to the over head tank of height 100 ft. Neglect all friction losses. Take specific gravity of the water as '1' and take efficiency of the pumps as 60%?**

Ans: Given Data

$$\text{Discharge (Q)} = 20 \text{ Gallons per minutes (GPM)}$$

$$\text{Depth of bore well} = 250 \text{ ft.}$$

$$\text{Height of the water tank} = 100 \text{ ft.}$$

$$\text{Specific gravity of water (S.G)} = 1.0$$

$$\text{Efficiency of the pump } (\eta) = 60\% = 0.6$$

$$\text{Pump capacity in Horse Power(HP)} = \frac{Q \times \text{Head} \times \text{Specific Gravity}}{3960 \times \eta}$$

Total Head = Depth of bore well + Height of the Tank

(in feet) = 250 + 100 = 350 Feet.

$$\begin{aligned}\text{Pump Capacity in HP} &= \frac{Q \times \text{Head} \times \text{Specific Gravity}}{3960 \times \eta} \\ &= \frac{20 \times 350 \times 1.0}{3960 \times 0.6}\end{aligned}$$